
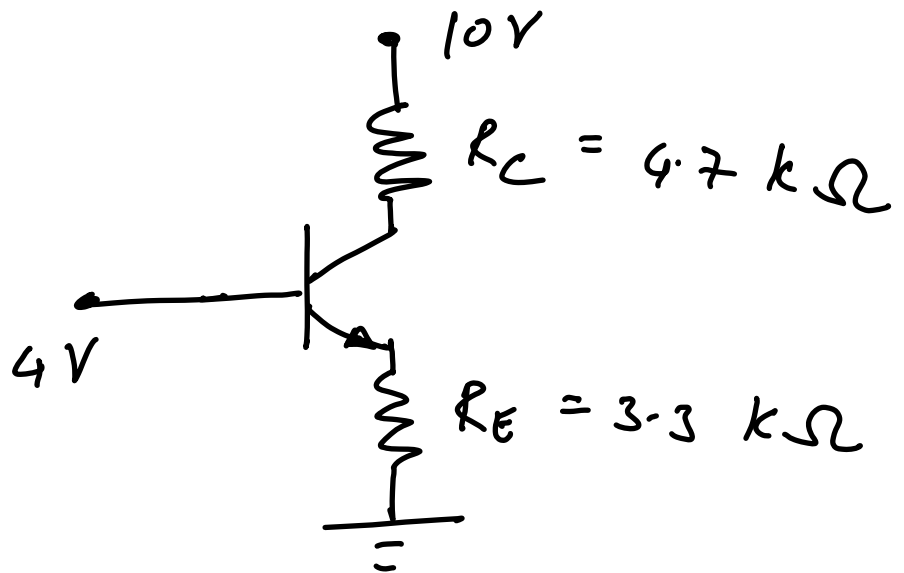


EXAMPLE 1

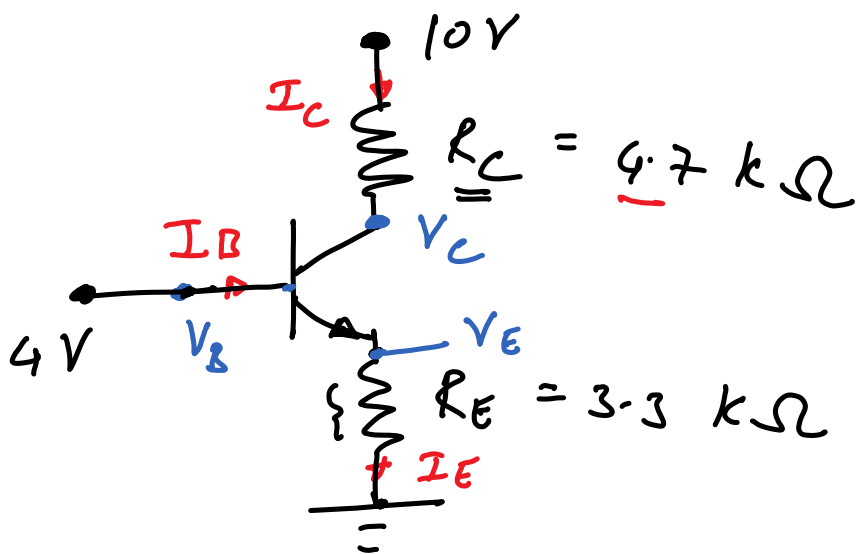

Compute V_C , V_E , V_B , I_E , I_B , I_C &
assume $\beta = 100$

Assume BJT is in active mode. We will check this assumption eventually.



$$10 - V_C = I_C R_C \quad \text{--- (1)}$$

$$4 - V_B = 0$$

$$\Rightarrow V_B = 4 \quad \checkmark$$

$$V_E - 0 = I_E R_E \quad \text{--- (2)}$$

$$\{ V_C, I_E, V_E, I_C \}$$

$$V_B - V_E = 0.7$$

$$4 - V_E = 0.7$$

$$V_E = 3.3 \text{ V}$$

$$I_C = \beta I_B \quad \text{--- (3)}$$

$$I_E = I_C + I_B \quad \text{--- (4)}$$

$$\underline{V_C}, \underline{V_E}, \underline{V_B}, \underline{I_C}, \underline{I_B}, \underline{I_E}$$

$$10 - V_C = I_C R_C \quad \text{--- (1)}$$

$$3.3 = I_E R_E \quad \text{--- (2)}$$

$$I_C = \beta I_B \quad \text{--- (3)}$$

$$I_E = I_C + I_B \quad \text{--- (4)}$$

$$V_C = 5.34 \text{ V}$$

$$I_E = 1 \text{ mA}$$

$$I_C = 0.99 \text{ mA}$$

$$I_B = 0.01 \text{ mA}$$

Check assumptions of active mode

$$I_B, I_C > 0 \quad V_{BE} = 0.7 \text{ V} ; I_C = \beta I_B$$


✓

assumed →

✓

$$V_C = V_C - V_E = 5.34 - 3.3 = 2.04 > 0.2$$

EXAMPLE 2

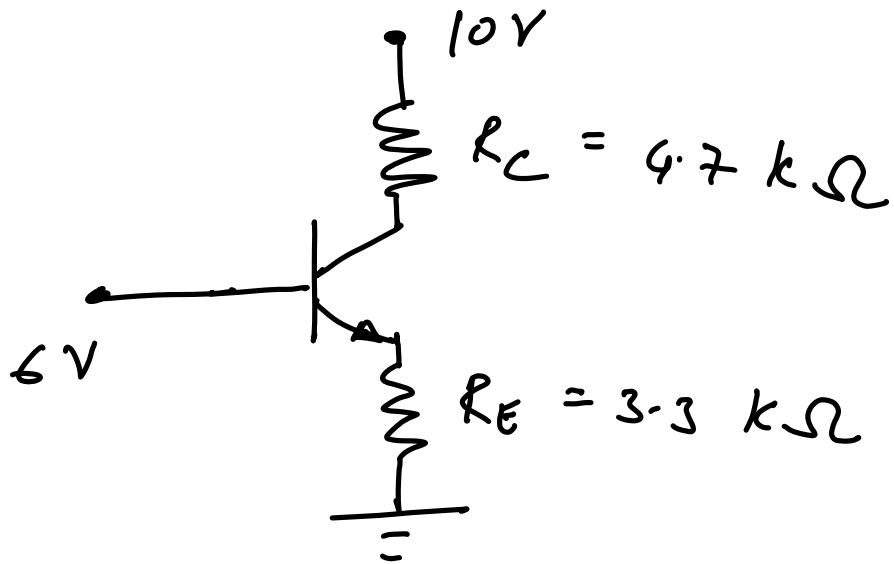

Check if the BJT is in active mode
($\beta = 100$)


Assumptions of active mode

$$\underline{I_C, I_B} > 0$$

$$\underline{V_{BE} = 0.7}$$

$$\underline{V_{CE}} \geq 0.2$$

$$\underline{I_C = \beta I_B}$$

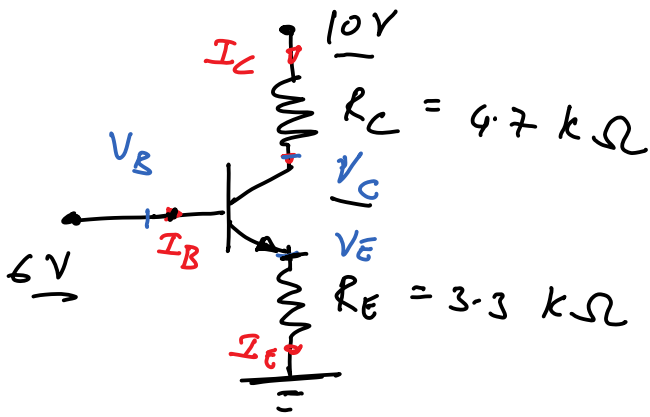

$$V_{CE} = V_C - V_E$$

$$= 2.25 - 5.3$$

$$= -3.05 \leq 0.2$$

(condition is false,
BJT is **NOT** in active mode)

$$V_{CE} = V_C - V_E = ?$$

$$\cancel{V_E} - 0 = I_E R_E$$

$$10 - V_C = I_C R_C$$

$$V_B = 6$$

$$V_{BE} = V_B - V_E = 0.7$$

$$6 - V_E = 0.7$$

$$\checkmark V_E = 5.3$$

Contd.


$$I_C = \beta I_B \quad ; \quad I_E = I_C + I_B$$

$$I_E = \frac{V_E}{R_E} = \frac{5.3}{3.3 \times 10^3} = 1.67 \text{ mA}$$

$$\left. \begin{array}{l} I_C + I_B = 1.67 \\ I_C = \beta I_B \end{array} \right\} \begin{array}{l} I_C = 1.65 \text{ mA} \\ I_B = 0.02 \text{ mA} \end{array}$$

$$10 - V_C = 1.65 (10^3) (4.7 \times 10^3) \Rightarrow V_C = 2.25$$

EXAMPLE 3

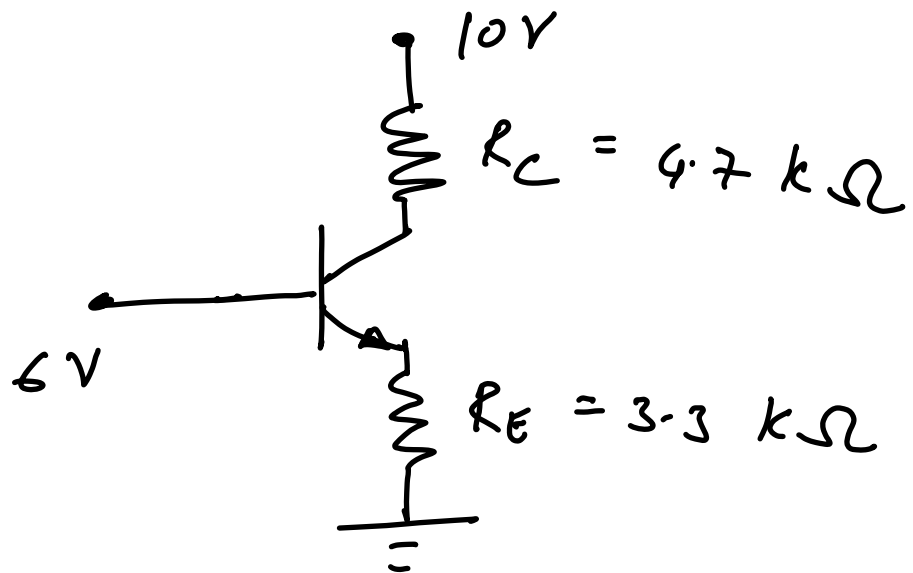

Compute $V_C, V_B, V_E, I_C, I_B, I_E$
assuming the BJT is in saturation
mode


In saturation mode

$$I_B, I_C > 0$$

$$V_{BE} \geq 0.7$$

$$V_{CE} \approx 0.2$$

$$I_C \neq \beta I_B$$

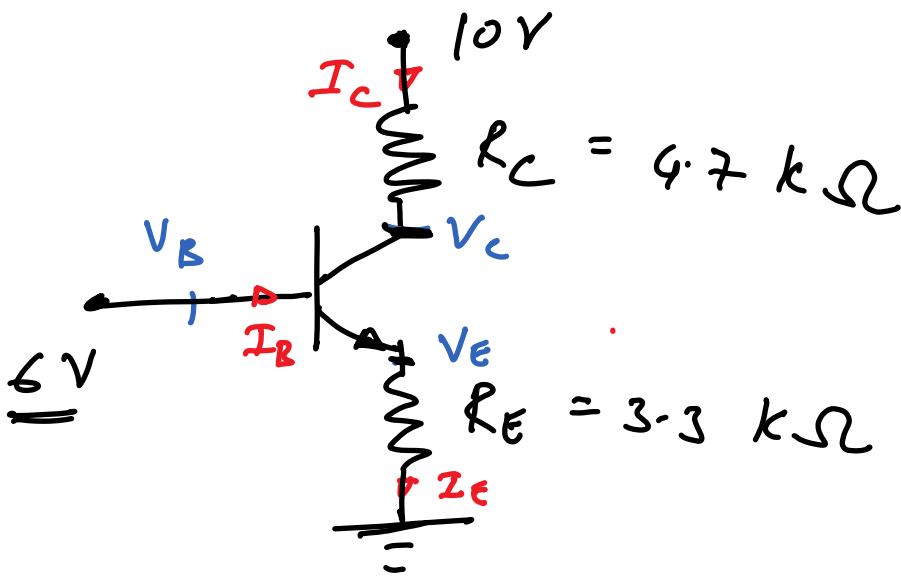

$V_B, V_C, V_E, I_C, I_B, I_E$

$$10 - V_C = I_C R_C \quad (1)$$

$$6 - V_B = 0 \quad (2)$$

$$V_E - 0 = I_E R_E \quad (3)$$

$$V_{BE} = V_B - V_E = 0.7 \quad (4)$$

$$V_{CE} = V_C - V_E = 0.2 \quad (5)$$

$$I_C = I_B + I_E \quad (6)$$

$$V_E = 5.3V$$

$$V_C = 5.5V$$

$$V_B = 6V$$

$$I_E = 1.6mA$$

$$I_B = 0.64mA$$

$$I_C = 0.96mA$$

$$\Rightarrow \frac{I_C}{I_B} = \frac{0.96}{0.64} = 1.5 \text{ (not } 100)$$

Saturation mode $\neq \beta$